

UNIVERSITEIT • STELLENBOSCH • UNIVERSITY jou kennisvennoot • your knowledge partner

E344 Assignment 3

Willem Viljoen 22877169

Report submitted in partial fulfilment of the requirements of the module

Design (E) 344 for the degree Baccalaureus in Engineering in the Department of Electrical

and Electronic Engineering at Stellenbosch University.



Plagiaatverklaring / Plagiarism Declaration

- 1. Plagiaat is die oorneem en gebruik van die idees, materiaal en ander intellektuele eiendom van ander persone asof dit jou eie werk is.
 - Plagiarism is the use of ideas, material and other intellectual property of another's work and to present is as my own.
- 2. Ek erken dat die pleeg van plagiaat 'n strafbare oortreding is aangesien dit 'n vorm van diefstal is.
 - I agree that plagiarism is a punishable offence because it constitutes theft.
- 3. Ek verstaan ook dat direkte vertalings plagiaat is.

 I also understand that direct translations are plagiarism.
- 4. Dienooreenkomstig is alle aanhalings en bydraes vanuit enige bron (ingesluit die internet) volledig verwys (erken). Ek erken dat die woordelikse aanhaal van teks sonder aanhalingstekens (selfs al word die bron volledig erken) plagiaat is.

 Accordingly all quotations and contributions from any source whatsoever (including the internet) have been cited fully. I understand that the reproduction of text without quotation marks (even when the source is cited) is plagiarism
- 5. Ek verklaar dat die werk in hierdie skryfstuk vervat, behalwe waar anders aangedui, my eie oorspronklike werk is en dat ek dit nie vantevore in die geheel of gedeeltelik ingehandig het vir bepunting in hierdie module/werkstuk of 'n ander module/werkstuk nie.

 I declare that the work contained in this assignment, except where otherwise stated, is my original work and that I have not previously (in its entirety or in part) submitted it for grading in this module/assignment or another module/assignment.

22877169	WIJA							
Studentenommer / Student number	Handtekening / Signature							
W. Viljoen	24 August 2021							
Voorletters en van / Initials and surname	Datum / Date							

Contents

Declaration List of Figures								
No	omenclature	v						
1.	Fuse	1						
	1.1. Literature	1						
	1.2. Design	1						
2.	Undervoltage battery protection	3						
	2.1. Literature	3						
	2.2. Overview	3						
	2.3. 5V rail	3						
	2.4. High-side switch	4						
	2.5. Voltage monitoring with hysteresis design	4						
	2.6. Circuit diagram	4						
	2.7. Results	4						
Bi	ibliography	5						
Α.	GitHub Activity Heatmap	6						
В.	. Social contract	7						

List of Figures

1.1.	Following the	graph of B	for blade	fuses: [1].	 					 _		_	1

List of Tables

Nomenclature

Variables and functions

 V_OC Open circuit voltage.

 I_SC Short circuit current P Power.

V Voltage. I Current.

 $P_M AX$ Maximum power.

 $V_M PP$ Voltage at maximum power point. $I_M PP$ Current at maximum power point.

C Battery's C-rating (4A).

 V_GS Gate-Source voltage of a NMOS. V_SG Source-Gate voltage of a PMOS.

 V_TH Threshold voltage of a MOSFET.

Acronyms and abbreviations

PV Photovotalic.

STC Standard Testing Conditions.

MPPT Maximum Power Point Tracker.

NMOS Negative-channel Metal-Oxide Semiconductor.

PMOS Pegative-channel Metal-Oxide Semiconductor.

MOSFET Metal-Oxide-Semiconductor Field-Effect Transistor.

Chapter 1

Fuse

1.1. Literature

The average temperature in South Africa is 27°C in according to weather-and-climate.com, but tests done by sustainable.org suggests that maximum temperatures of 40°C is reached during summertime Considering that the circuit will be mounted on a rooftop within a casing where components such as resistors and operational amplifiers also resides, it is viable to assume that temperatures of up to 50°C can be reached. The operating temperature of the battery also suggests that the circuit should be kept under 50°C. The RS-pro fuse is affected by ambient temperature, and this parameter should therefor be considered when choosing an applicable fuse. The battery discharge rate, according to docs.rs should not exceed 1.85V/cell and 2.36A when discharged over a 45 min period. This should also be considered when choosing the fuse. Considering that the circuit will not exceed 1A of current under normal load conditions, a viable fuse can be chosen.

1.2. Design

Assuming that a maximum temperature of 50°C will be reached, the following calculation can be made: According to littlefuse.com, Catalog Fuse Rating = $\frac{NormaloperatingCurrent}{0.75 \times PercentofRatingattemperature}$. Considering a normal operating current of 1A at 50°C (Worst case scenario): $\frac{1}{0.75 \times 0.96} = 1.4$

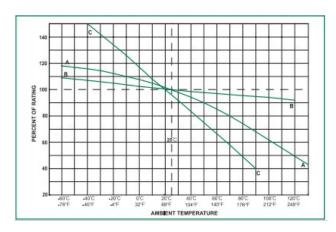


Figure 1.1: Following the graph of B for blade fuses: [1].

A. A fuse of at least 1.4A is needed, considering that a fuse smaller than this will blow with normal operation. The fuse size must therefor be in the range of 1.4A to 2.36A to protect the

battery without blowing under normal operation. Therefor I have chosen to use the RS-pro $2\mathrm{A}$ Fuse.

Chapter 2

Undervoltage battery protection

This chapter answers the question: "Did the student follow a systematic approach to design the sought solution?". You therefore need to follow a systematic/logic path, and did you clearly communicate it.

2.1. Literature

Here you can include stuff you learnt that you will use in the design - e.g. operational amplifiers as comparators, hysteresis, rail-to-rail comparators. If you feel there was nothing you had to learn to do this, feel free to leave this section out.

2.2. Overview

The undervoltage protection principle is based on the circuit protecting the battery against deep discharge, this discharge is known as the discharge below the minimum voltage and load against the given undervoltage. After discharging a battery to the lowest supply voltage circuit disconnects the load from the battery and does not draw any current. Undervoltage protection is applicable for the protection of batteries such as lead-acid (Pb), NiCd, NiMH, Li-Ion and Li-Pol accumulators. The important weaknesses that the batteries must be protected from are overvoltage conditions because it can place the batteries in a dangerously unpredictable state. The equivalent is valid for undervoltage conditions. Therefore, undervoltage protection is frequently only included in the primary layer of protection, but not the secondary layer. In the greatest given case, when the voltage falls only marginally below the minimum, there will be a small loss in capacity and the self-discharge rate will rise. The smaller the cell voltage gets, the more prominent these effects become. If the cell voltage gets too low, then it grows to be hazardous to try and attempt to recharge the cell because it may create a short and involve severe damage to its environments.

2.3. 5V rail

Here explain your selection of 5V regulator.

2.4. High-side switch

Here you describe the design choices made for the switch (Note, this is not the switch we use to control the LM317 output, it is similar switch that controls the supply from the battery to the same regulated line, but it does not have a blocking diode).

2.5. Voltage monitoring with hysteresis design

Explain your design of the comparator with hysteresis, taking into account things like common mode voltages, differential voltages, input-to-rail voltages, hysteresis deadband, resistor values and current consumption, etc.

2.6. Circuit diagram

Show your circuit diagram (the one you will submit). Ensure that it is of good quality, and preferably a vector (metadata) plot, not a raster (pixel) plot, so you can zoom in and select text from it.

2.7. Results


Here you include your simulation results and your measured results. For the measured results, it would be most beneficial to show on the same oscilloscope screen-grab (or CSV plot), how the switch went through the stages of the hysteresis loop (similar to what you had to do for the video). You are welcome to use subplots to save space.

Bibliography

[1] BBC, "How to make opamps amp op," 2018. [Online]. Available: www.electronics-tutorials. ws

Appendix A

GitHub Activity Heatmap

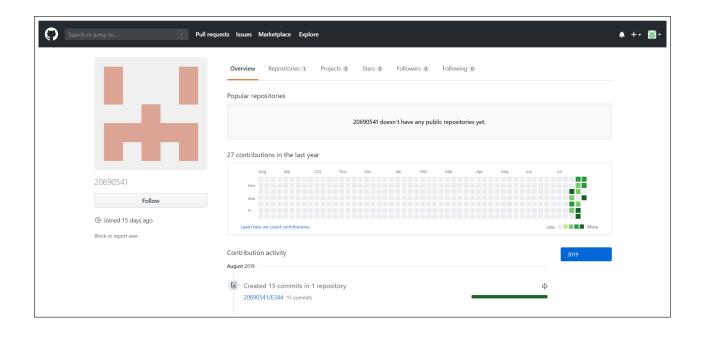

Appendix B

Social contract



E-design 344 Social Contract

2021

The purpose of this document is to establish commitment between the student and the organisers of E344. Beyond the commitment made here, it is not binding.

In the months preceeding the term, the lecturer (Thinus Booysen) and the Teaching Assistant (Kurt Coetzer) spent countless hours to prepare for E344 to ensure that you get your money's worth and that you are enabled to learn from the module and demonstrate and be assessed on your skills. We commit to prepare the assignments, to set the tests and assessments fairly, to be reasonably available, and to provide feedback and support as best and fast we can. We will work hard to give you the best opportunity to learn from and pass analogue electronic design E344.

I acknowledge that E344 is an important part of my journey to becoming a professional engineer, and that my conduct should be reflective thereof. This includes doing and submitting my own work, working hard, starting on time, and assimilating as much information as possible. It also includes showing respect towards the University's equipment, staff, and their time.

Prof. MJ Booysen Student number: 228777169.

Signature: Signature: Signature: Signature: Date: 16 Aug 2021

Date: Date: 16 Aug 2021

1